EISCAT's High Power HF radar

Technical description and user instructions

MTR, 20190805

This describes the hardware and software used to operate the high power HF radar as of about 2016, using Array-3 as an array of 12 receiving antennas, and one or more transmitters in Array-1 for transmission. The physical frequency range is thereby limited to 5.4 to 8.0 MHz. The 12 receiving antennas on Array-3 are the 6 east-west-aligned rows of 6 crossed full wave dipoles. The 12 specially-modified coaxial switches (S23 which is the name used in various documentation figures and on the cables used to control these switches) have an N-connector output connected to the inner conductor from Array-3 whenever that switch is in the position connecting the transmitter to Array-2. See the document '**TRswitch_instructions.odt**' and .pdf on how the coaxial switch was modified.

Twelve equal length (ca. 70m) RG213 coaxial cables connect each S23 Rx/Tx switch output to the receiver hardware inside the transmitter hall, on the south wall between Tx1 and Tx3. After passing through some isolating coaxial relays (isolator), pin-diode receiver protector switches (RxProt) and low pass (LP) filters, the signal goes to 6 USRP-200N receivers, each of which has two input

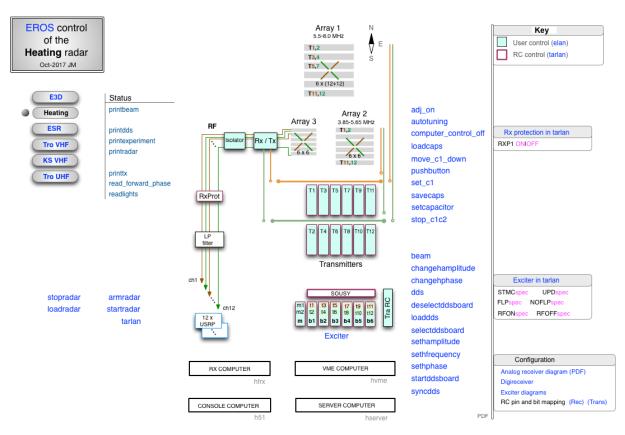


Figure 1 Schematic diagram of the Heating system, showing some of the EROS commands used to control various parts of the hardware (from <u>http://www.sgo.fi/~jussi/eiscat/erosdoc/index.html</u>)

channels RF1 and RF2, giving 12 channels. Fig.1 (from Jussi Markkanen) shows these items schematically. The rest of the hardware in the transmitter hall is shown in Figure 2.

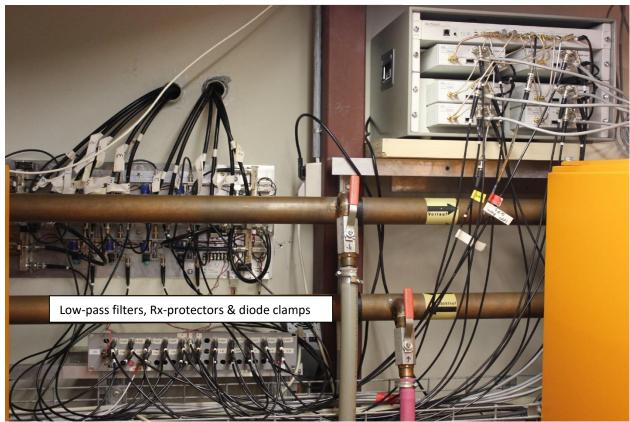


Figure 2 Receiver hardware: Rx-isolator, Rx-protector, and USRP receivers on south wall of transmitter hall, between Tx1 and Tx3.

Several protective measures have been built into the system, to ensure that the USRP receivers and associated hardware are not damaged by too high HF radio wave levels from the heating transmitters. First there are the modified **Tx/Rx coaxial switches** which make the connection to the inner conductor of the 10cm aluminium coax to/from Array-3 only when the connection from the transmitter is made to Array-2. However, transmission on Array-2 during the radar operation are not desirable because that array is so close to Array-3 that the RF levels are very high, and furthermore they are mostly on the wrong frequency range for radar use. So there is an interlock system which disconnects the receiving antennas from the receiver system, called the **receiver isolator**, whenever any transmitter is not connected to array-1. This system is a set of 12 coaxial relays mounted on a plate on the wall of the transmitter hall where the RG213 cables come in (see Fig.2).

The individual items and their controls are now described individually in more detail.

Slow Tx/Rx coaxial switches

See the document '**TRswitch_instructions.odt**' and .pdf on how the original coaxial switch was modified to provide a receiver signal.

These switches are under pushbutton control. The Eros command for transmitter 1 is: **pushbutton t1 a3** (or a2 or a1). When the transmitter is not connected to a3, the receiver port is automatically connected to that antenna row. Fig. 3 shows one of the coaxial switches, with the N-connector for the receiver output.

Receiver Isolator coaxial relays

All 12 isolator relays receive a common enable/disable signal. The function is to isolate all the antenna rows from the receiver whenever any transmitter is not connected to array-1. The interlock logic is done by a hardware modification in the 'coax-Zentrale' rack. In addition, an enable signal must be given from EROS with the command '**pushbutton t0 cn**' or 'hall **cn**', where **cn** is Guttorm's way of commanding 'coax relay on' and **cf** disables the relay. This cn command sends 24Vdc via the '**receiver isolator controller card**' (see Fig.3 and schematic in Fig. A1) in the 'coax-Zentrale' rack to the relay board on the wall at the other end of the transmitter hall. This controller card

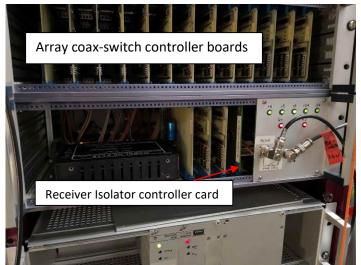


Figure 3 Receiver Isolator controller card in 'Coax-Zentrale' rack, with BNC input and output for the 'cn' / 'cf' control signal.

disables the 24Vdc if any transmitter is not in position Array-1. The philosophy behind this relay is that it is a much more robust relay than the later pin diode switch so that the rather large RF voltages induced (10's of volts) on an array-3 antenna row by any transmission on the nearby array-2 or another part of array-3 will not damage the pin-diode switches or the USRP. Transmissions on array-1 are off course allowed and desired in a radar mode, that array being further away and distributed over a larger area.

Receiver Protector

After the isolator relays, the signals go to pin-diode switches which are controlled by a single radar-controller bit via an optical fibre interface for radar operations. The switches are of type Mini-Circuits ZX80-DR230+ absorptive SPDT, with data sheet <u>ZX80-DR230+.pdf</u>. The TARLAN command is:

TARLAN command is

'RxP1 ON' or OFF

The receiver protectors and the following low-pass filters and diode clamps are inside a re-used 17" rack unit shown in Fig.4.



Figure 4. Rack unit containing receiver protectors, low-pass filters and diode clamps.

Low-pass Filters and diode clamps

After the receiver protectors anti-aliasing filters remove components above 10.7 MHz. Each channel has a Mini-Circuits BLP-10.7+ low pass filter installed (see Figs. 4 and A.4). The characteristics are described in data-sheet <u>BLP-10.7+.pdf</u>. They are followed by two back-to-back signal diodes to clip any high voltage signals before going to the USRP's via output BNC's on the front.

Notching stubs (optional)

When the HF radar is to be used simultaneously with some heater transmitters for heating, as in some PRAM experiments, then the heater wave may be too strong for the receiver system. The heating frequency would normally be different from the HF radar frequency and then the heater frequency can be attenuated by about 20-22 dB using a quarter wave coaxial cable as a stub. This open-ended cable acts as a notch filter, but has a relatively wide bandwidth such that the HF radar frequency is also likely to be attenuated, but somewhat less (like 3 dB for a radar frequency of 7.953 MHz with a stub cut for 6.2 MHz). Twelve stubs were made for the July 2019 PRAM experiments, and a typical transfer characteristic is shown in Fig. A. 5 They are joined to the output signal BNC's from the rack using a BNC T-piece.

USRP receivers

The input to each USRP should not exceed 2Vpp, which is why we put the protective measures above in place, with the diode clamps being the final device. Each USRP is started using the GNU Python script **thor.py**.

The EROS command is: usrp <command name>

These commands are still under development


Appendix

The schematic layout of the receiver isolator, receiver-protector and associated circuitry are shown in these sketches (Figures A.1-A.3):

RECEIVER ISOLATOR
Kunsteen solverstan
From A3 TO T/R
NX
Conx relay
J
One each for Rx 1-12
+12V (approx. 3 A)
For Bonholler
A 3 x 12 Coax relay Solenoids
777
Controller output is currently OV for "isolate" (relays OFF)
or + 5V for "enable" (relays ON). The 7405 has 5
spire gates - it can easily be reconfigured for neversed
Levels ar open - collectur output.
The isolatur board could optionally feature a manual
Switch to overvide the Control and enable the relays
but this should be hard to operate!

Figure A. 1 Receiver Isolator circuit.

	RECEN	ER ISOLATOR	CONTROLLER	2016-08-02	20190805 2016-08-04
	326			200 0,000	2016-08-04 (AS/MTR)
<u></u>	32a > >	+5V		+51 +1 1	
		-		10 #F 1 1	$\frac{1}{7}$
	1a - 1c>	S GND	·	GND	
			-T+2A	-	IONF
			Пік		
1.		7414	116		· · · · · · · · · · · · · · · · · · ·
*6]	220 >	64 GY 12	L A		· · · · · · · · · · · · · · · · · · ·
+12	210 > 11	50 55 10	 J		
L H	200 - 9	4 4 8	++		+SV
	1	14 17 2			T
10.5					
×9 d		2A 27 4	K		<u> </u>
	17a > 5	3A 3Y 6	I Y	9 13 0.0.	12
70	16a - 13 T	A 6V-12	c	GIA 64	
5 8		A 54 10	6		
			2		I LINA
*4 8		HA 47 8		74057	7405
3 .		A 37 6			
Tx2	124 >3	A 24 4	D		<u></u> +5∨
TxI	110	AIYL	F		2 0 0
	-	74:4	74133		-
			, , , , , , , , , , , , , , , , , 	30	L,5C
	M	-7			-!!
		-	M -1	BN	O BNC
		· · · · · · · · · · · · · · · · · · ·			
	Output is	logic high	shan all	S2 COax Shatch	es are
•		· •	no transmitter		H2 or A3).
		•			
	100,4	•			· · · · · · · · · · · · · · · · · · ·
					······································
		TIONE			· · · · · · · · · · · · · · · · · · ·
		77	t		· · ·
	LC filter on	each input	· · · · · · · · · · · · · · · · · · ·		-
	ceiver Isolator				
oller, sch	ematic and PC boo	ird			
		10 March 10		A REAL PROPERTY OF A REAL PROPER	CONTRACTOR OF THE PARTY OF THE PARTY

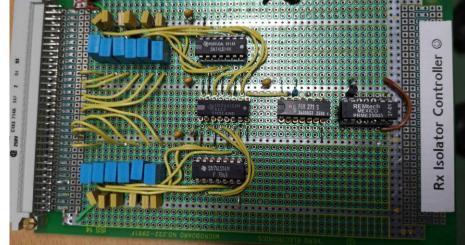

	T/R SL			X80- DR	Darch			
	,1	<u> </u>	~~~ ,	1	46-2+			
	RF1'	T J SOR		1 ,		-		
	1 1	<u> </u>		COM			· · · · · · · · · · · · · · · · · · ·	To US
From Rx isolator	1		7		$f \rightarrow f$		>	Input
RX 130	es-		<u> </u>	1		- \$ \$		
		7	Soc -	1		'		
	1	5 SOR	I	1				
	1	11 11	,	1		ſ	7	to si
	+51		-		RXP	Logic		Cantro
		11 2	2 17		fibre from			
			,		#/c			
		Control						
The Z	<u> 180 -</u> DR23	0-S+ (Control	inputs	should	be s	intered	
as foll				•				
			- 18		Control 1	IP3		
Ma						2		
Rx er	abled	3			H	L		
Rx pr	tected	<u> </u>			· · ·	,		
		L Contra						
to avoi	us natio	Le Contra Compling	5_into	, the	Signal	par		
to avoi	us natio	. complete	5_into	, the	Signal	par		
to avoi	nal, ar	. complete	beth	en si	Signal po	path other,	a~ p	nodu leti
to and the sign Later	nal, ar	compling compling	betu to	en si	Signal po The S	poth the .	or r	the
to and the sign Later RF2	is note mal, or we mini-	compling compling gut wont This is	bethe to	add chage	Signal prod po The s	path the . incling Rx en	or r tra	the prode
the sing the sing Later RF2 to use	is notice maly or use mi uput. State	compling compling ght want This want	betu betu to to	add charge	Signal po grad po The so the so	path otho, incling Rx en he to	or r Vis alled row	the prode
to and the sign Later RF2 to use 12 pai	id note mal, or ure mi nput. State	compling compling ght croat This c 2.	to beth to mult the con	add change to a	Signal po grad po The so the so	path otho, incling Rx en he to	or r Vis alled row	the prode
to and the sign Later RF2 to use 12 pai	id note mal, or ure mi nput. State	compling compling ght want This want	to beth to mult the con	add change to a	Signal po grad po The so the so	path otho, incling Rx en he to	or r Vis alled row	the prode
to and the sign Later RF2 to use 12 pai	id note mal, or ure mi nput. State	compling compling ght croat This c 2.	to beth to mult the con	add change to a	Signal po grad po The so the so	path otho, incling Rx en he to	or r Vis alled row	the prode
to and the sign Later RF2 to use 12 pai Charge	id niche mal, ar ure mi nput. State rs of Con be	compling compling girt wont This is a	to bethe mult to conside eosite	add change to a y!	Signal grad po The Se able Se Commo	path otho. incling Rx cn rec per	or r tris ailed row	The The Mode te all This
to and the sign Later RF2 to use 12 pai Charge	id netse mal, or ure mi nput. State rs of Con be	compling compling ght want This want and in number Power her	to bethe to to to to to to to to to to to to to	the charge charge to a y! of 2:	Signel gried po Tx S in the educ Se Common K80- DRD	path stho, incling Rx en re to So-S+	or r via abled row at So	the the prode this this
to and the sign Later RF2 to use 12 pai Charge	id nation mal, or use mi nput. Statz Con be - 1. issue	compling compling ght want This w of	to bethe mult for the cosily cosily the cosily	the change change to a y! is terr	Signel grid po Tx S the elle Se Connor KQD-DRD ninted	path stho. anoling Rx en he to point 30-S+ in an	alled row	the the prode this be an d (bad
to and the sign Later RF2 to use 12 pai Charge	id nation mal, or use mi mput. Statz con be - 1. issue 2.	compling compling ght want This is 2. I control in nucle Power has when an The T/R	to bethe to to to to the Sinte	the strees signals add changed to a y! of 2: is term ch als	Signel pred po The the elle Se Common KQD - DED nineted is not	path stho. inveling Rx en he to point 30-5+ in an adducts	or r vis alled row alled row star	The The Mode to all This be an al (bad issue
to and the sign Later RF2 to use 12 pai Charge	in nehe mal, or une mi nput. State rs of Con be - 1. issue 2. of 'p	compling compling ght want This want an in control in nucle Power has in an The T/R ram' type	to bethe multip to control ecosite thing toman Sunte e Con	the charge charge charge to a to a y! of 2: is terv chard do rescue charge to a	Signel grid po Tx S the edu Se Commo K90 - DE2 niceted heating	path tho, incling Rx en the point SO-S+ in an address / radar	or r via abled now at Sb may intern the experi	the the mode the all this be an al (bad issue inarts
to and the sign Later RF2 to use 12 pai Charge	id nation mal, or use mi nput. Stati rs of Con be - 1. issue 2. of p the Tx	compling compling ght wont This wont This wont of the control in made Power has wonde Power has wonde The T/R ram type s may	to besture to to to to to to to to to to to to to	the the star add charge the the the the the the the th	Signel grid po Tx S the elle Se Common K80-DRD ninted us not heating duing	path stho. anoling Rx en fe to point 30-St in an address / radar	or r via alled row at so intern intern the experi receptio	the the prode this this be an issue inerts n.
to and the sign Later RF2 to use 12 pai Charge	id nation mal, or use mi nput. Stati rs of Con be - 1. issue 2. of p the Tx	compling compling ght want This want an in control in nucle Power has in an The T/R ram' type	to besture to to to to to to to to to to to to to	the the star add charge the the the the the the the th	Signel grid po Tx S the elle Se Common K80-DRD ninted us not heating duing	path stho. anoling Rx en fe to point 30-St in an address / radar	or r via alled row at so intern intern the experi receptio	the the prode this this be an issue inerts n.

Figure A. 3 Receiver protector (T/R) switch (solid state)

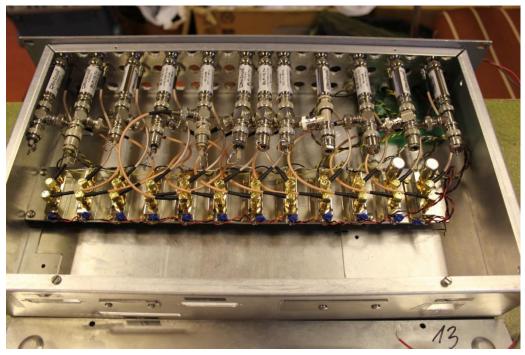


Figure A. 4 Receiver Protector and low-pass filter box.

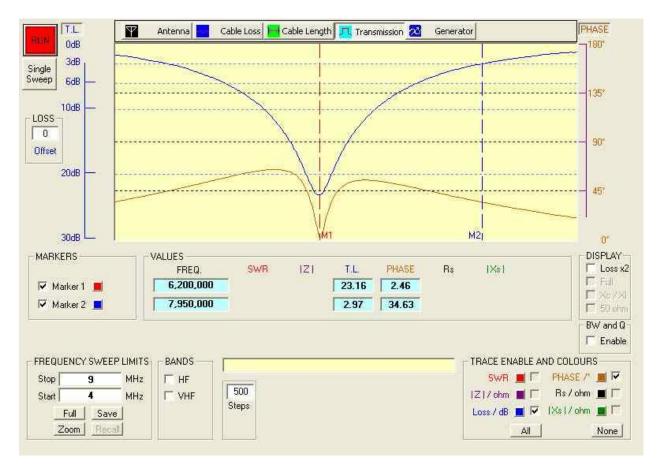


Figure A. 5 Transmission curve for a quarter wave stub for 6.2 MHz, measured with MiniVNA network analyser.